



# PLC Lab Test


Name: Kshitij Kumar Sharma

Roll no: 1905514

Branch: CSE

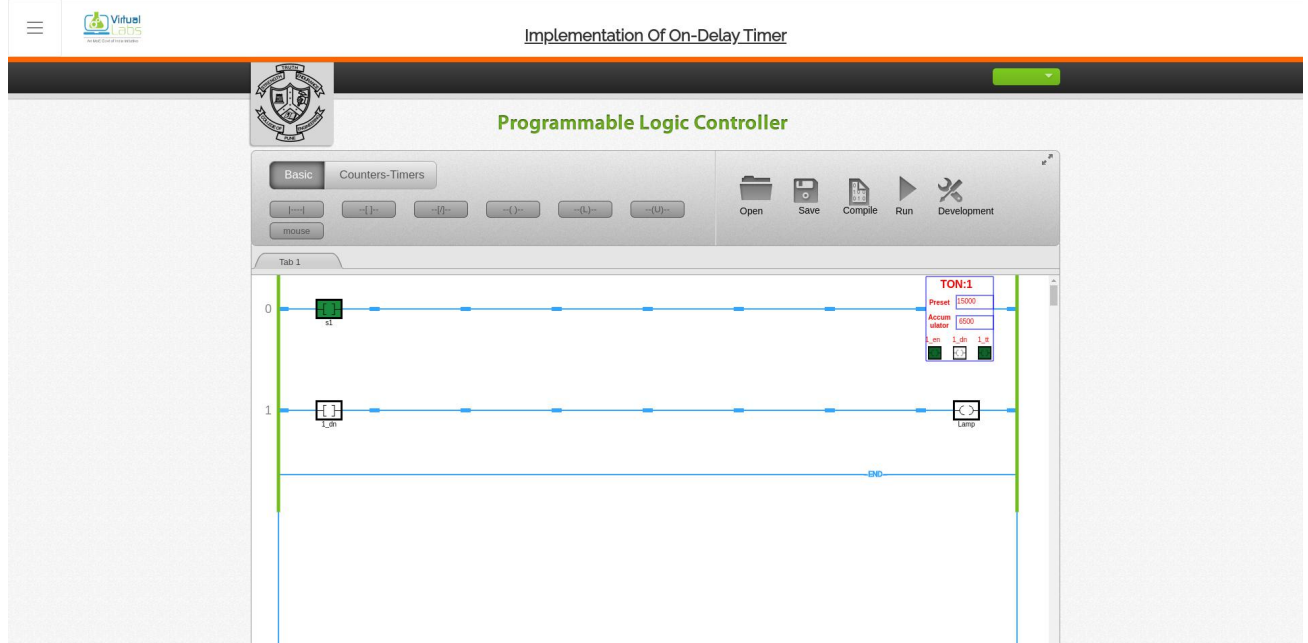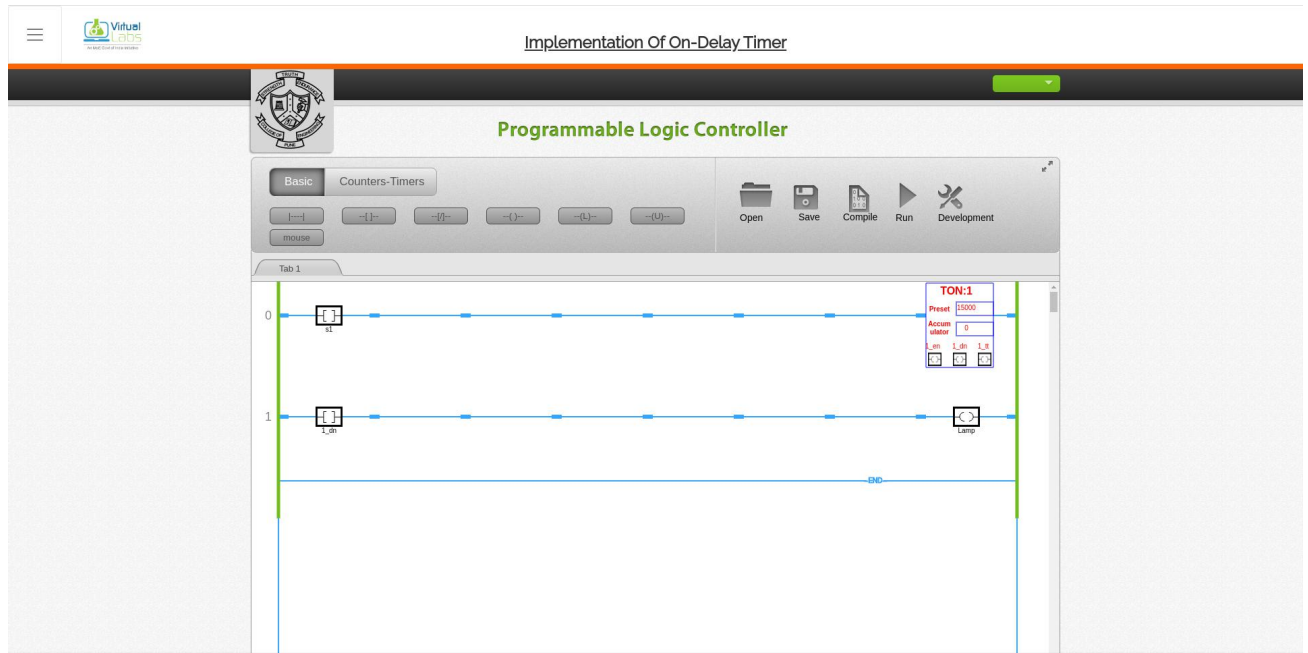Q1. Write a ladder Program when the lamp should glow after a delay of 15 second when start switch s1 is made on. The lamp should remain in glowing condition till the start switch s1 is made off. The lamp should go immediately off when start switch s1 is made Off.



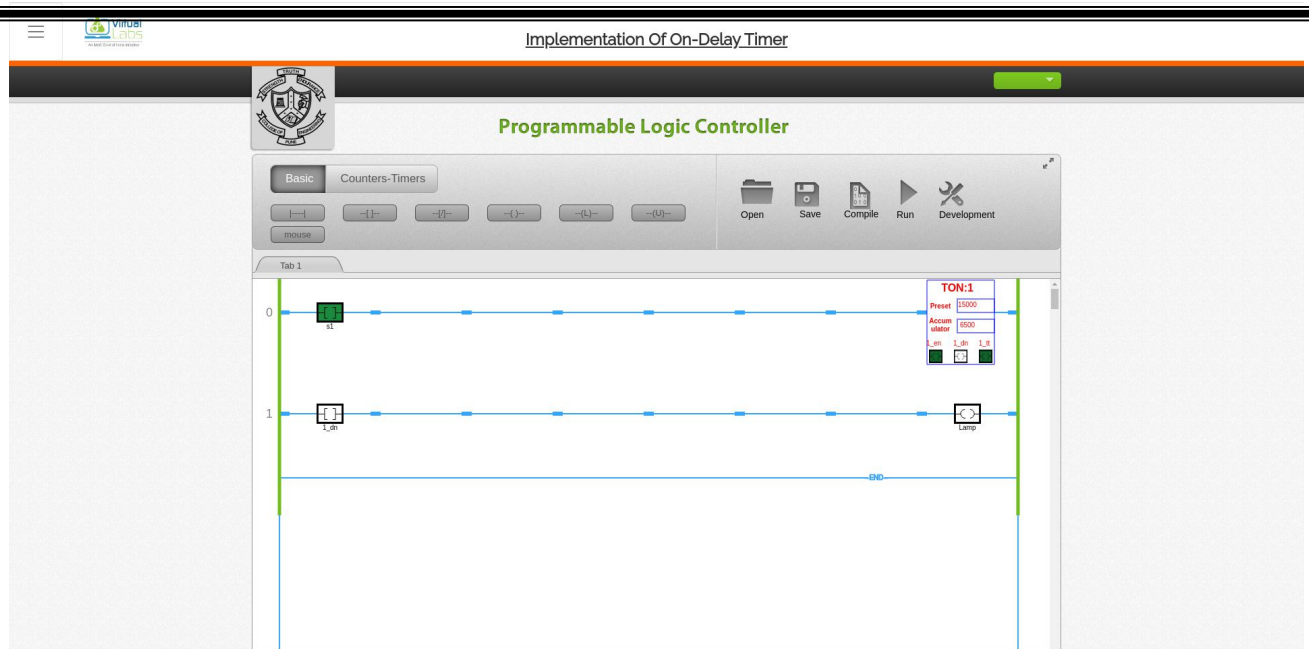

Q3. Write a ladder Program such that The lamp should glow when either the switch (S1 & S2) or S3 is ON.

